

# Combinational Logic

Jia Chen  
jiac@ucr.edu

*Slides adopted from Hung-Wei Tseng*

# Outline

- Two types of logics
- The **theory** behind combinational logics
- The building blocks of combinational logics

# Types of circuits

# Combinational v.s. sequential logic

- Combinational logic
  - The output is a pure function of its current inputs
  - The output doesn't change regardless how many times the logic is triggered — Idempotent
- Sequential logic
  - The output depends on current inputs, previous inputs, their history

# When to use combinational logic?

- How many of the following can we simply use combinational logics to accomplish?

- ① Counters
- ② Adders
- ③ Memory cells
- ④ Decimal to 7-segment LED-decoders

A. 0

B. 1

C. 2

D. 3

E. 4

# When to use combinational logic?

- How many of the following can we simply use combinational logics to accomplish?

- ① Counters — You need the previous input
- ②✓ Adders
- ③ Memory cells — You need to keep the current state
- ④✓ Decimal to 7-segment LED-decoders

A. 0

B. 1

C. 2

D. 3

E. 4

# Theory behind each

- A **Combinational logic** is the implementation of a **Boolean Algebra** function with only Boolean Variables as their inputs
- A **Sequential logic** is the implementation of a **Finite-State Machine**

# Boolean Algebra



# Boolean algebra

- Boolean algebra — George Boole, 1815—1864
  - Introduced binary variables
  - Introduced the three fundamental logic operations: AND, OR, and NOT
  - Extended to abstract algebra with set operations: intersect, union, complement

# Basic Boolean Algebra Concepts

- $\{0, 1\}$ : The only two possible values in inputs/outputs
- Basic operators
  - AND ( $\cdot$ ) —  $a \cdot b$ 
    - returns 1 only if both a **and** b are 1s
    - otherwise returns 0
  - OR ( $+$ ) —  $a + b$ 
    - returns 1 if a **or** b is 1
    - returns 0 if none of them are 1s
  - NOT ( $'$ ) —  $a'$ 
    - returns 0 if a is 1
    - returns 1 if a is 0

# Truth tables

- A table sets out the functional values of logical expressions on each of their functional arguments, that is, for each combination of values taken by their logical variables

## AND

Input		Output
A	B	
0	0	0
0	1	0
1	0	0
1	1	1

## OR

Input		Output
A	B	
0	0	0
0	1	1
1	0	1
1	1	1

## NOT

Input	Output
A	
0	1
0	1
1	0
1	0

# Let's practice!

- $X, Y$  are two Boolean variables. Consider the following function:

$$X \cdot Y + X$$

How many of the following the input values of  $X$  and  $Y$  can lead to an output of 1

①  $X = 0, Y = 0$

②  $X = 0, Y = 1$

③  $X = 1, Y = 0$

④  $X = 1, Y = 1$

A. 0

B. 1

C. 2

D. 3

E. 4

# Let's practice!

- X, Y are two Boolean variables. Consider the following function:

$$X \cdot Y' + X$$

How many of the following the input values of X and Y can lead to an output of 1

①  $X = 0, Y = 0$

②  $X = 0, Y = 1$

③  $X = 1, Y = 0$

④  $X = 1, Y = 1$

A. 0

B. 1

C. 2

D. 3

E. 4

Input					Output
X	Y	Y'	XY'	XY' + X	
0	0	1	0	0	0
0	1	0	0	0	0
1	0	1	1	1	1
1	1	0	0	1	1

# Derived Boolean operators

- NAND —  $(a \cdot b)'$
- NOR —  $(a + b)'$
- XOR —  $(a + b) \cdot (a' + b')$  or  $ab' + a'b$
- XNOR —  $(a + b') \cdot (a' + b)$  or  $ab + a'b'$

**NAND**

Input		Output
A	B	
0	0	1
0	1	1
1	0	1
1	1	0

**NOR**

Input		Output
A	B	
0	0	1
0	1	0
1	0	0
1	1	0

**XOR**


Input		Output
A	B	
0	0	0
0	1	1
1	0	1
1	1	0

**XNOR**

Input		Output
A	B	
0	0	1
0	1	0
1	0	0
1	1	1


# **Express Boolean Operators/Functions in Circuit “Gates”**
 
# Boolean operators their circuit “gate” symbols







# How to express $y = e(ab+cd)$

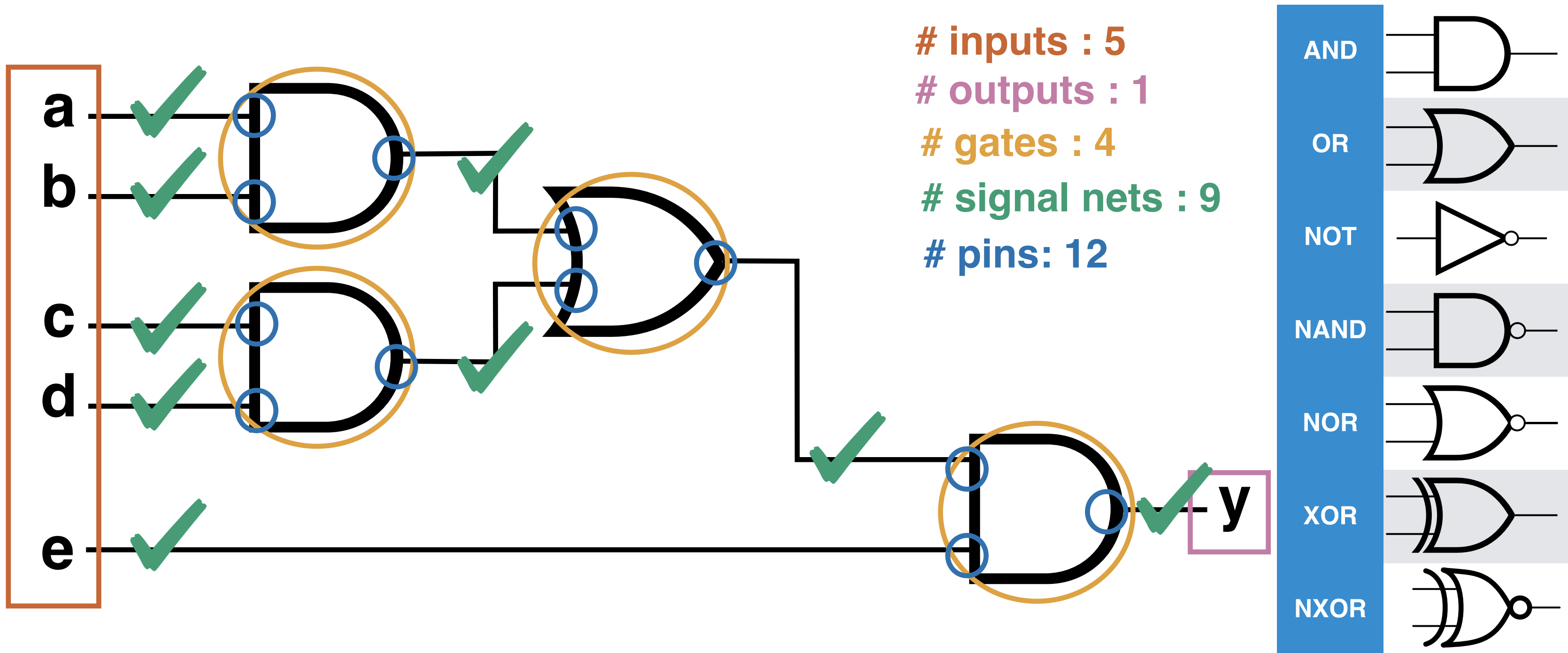


# We can make everything NAND!

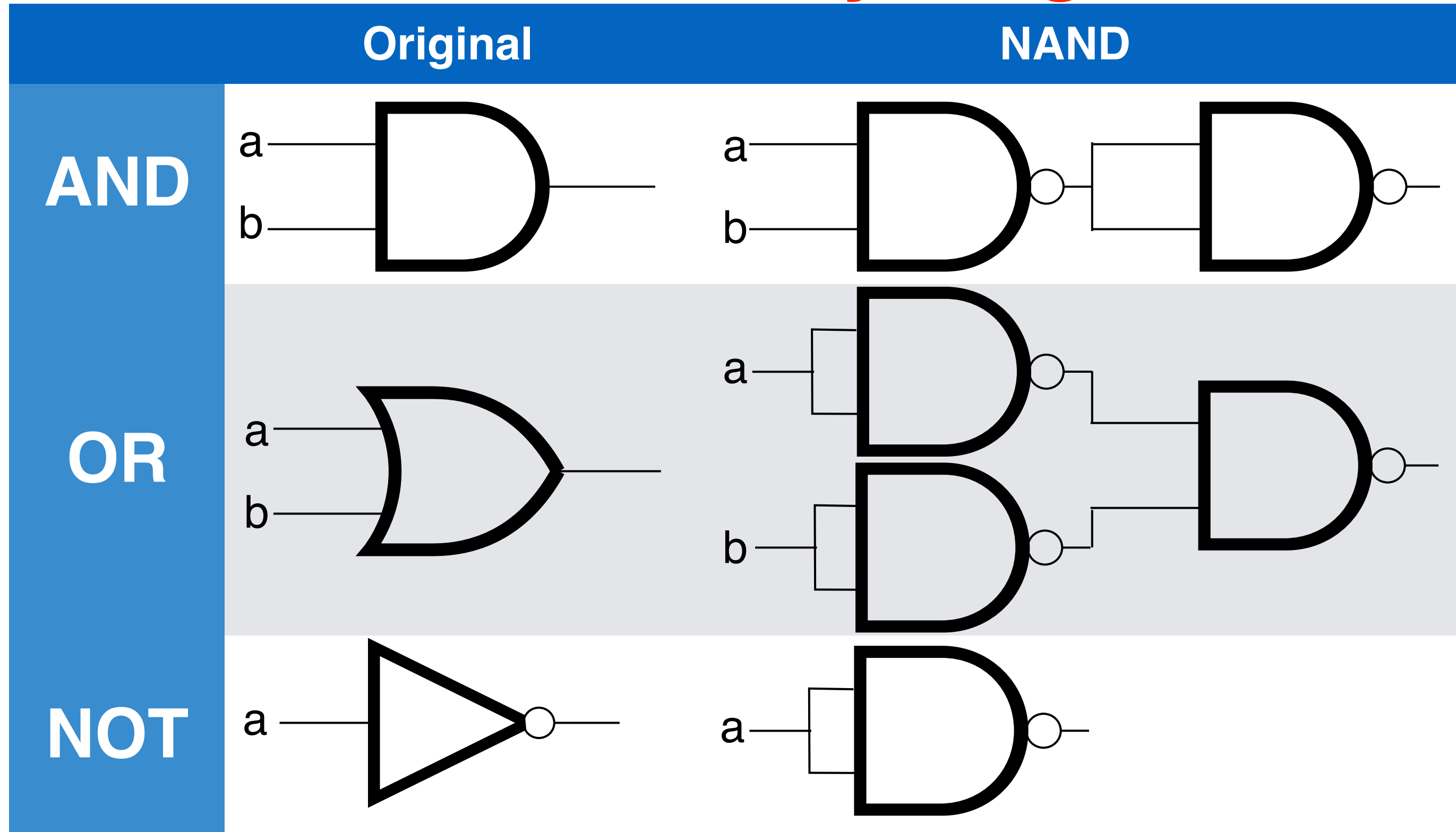


# We can also make everything NOR!

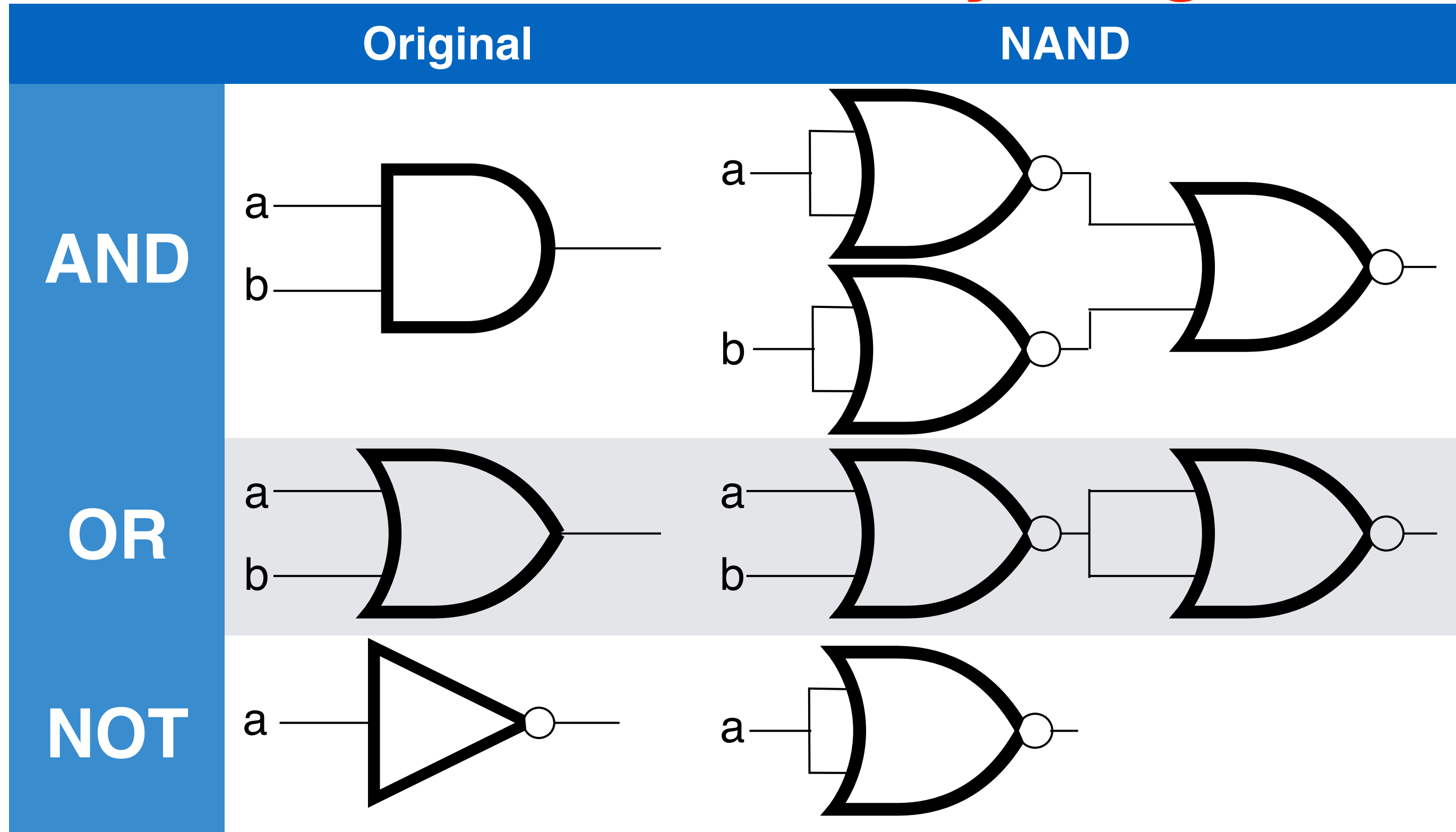

**How to express  $y = e(ab+cd)$**

 

**How to express  $y = e(ab+cd)$**

 


# How gates are implemented?
 
# Two type of CMOSs


- nMOS

- Turns on when  $G = 1$
- When it's on, passes 0s, but not 1s
- Connect S to ground (0)
- Pulldown network




- pMOS

 - Turns on when  $G = 0$
- When it's on, passes 1s, but not 0s
- Connect S to Vdd (1)
- Pullup network




# NOT Gate (Inverter)

Input	NMOS (passes 0 when on G=1)	PMOS (passes 1 when on G=0)	Output
A			
0	OFF	ON	1
1	ON	OFF	0

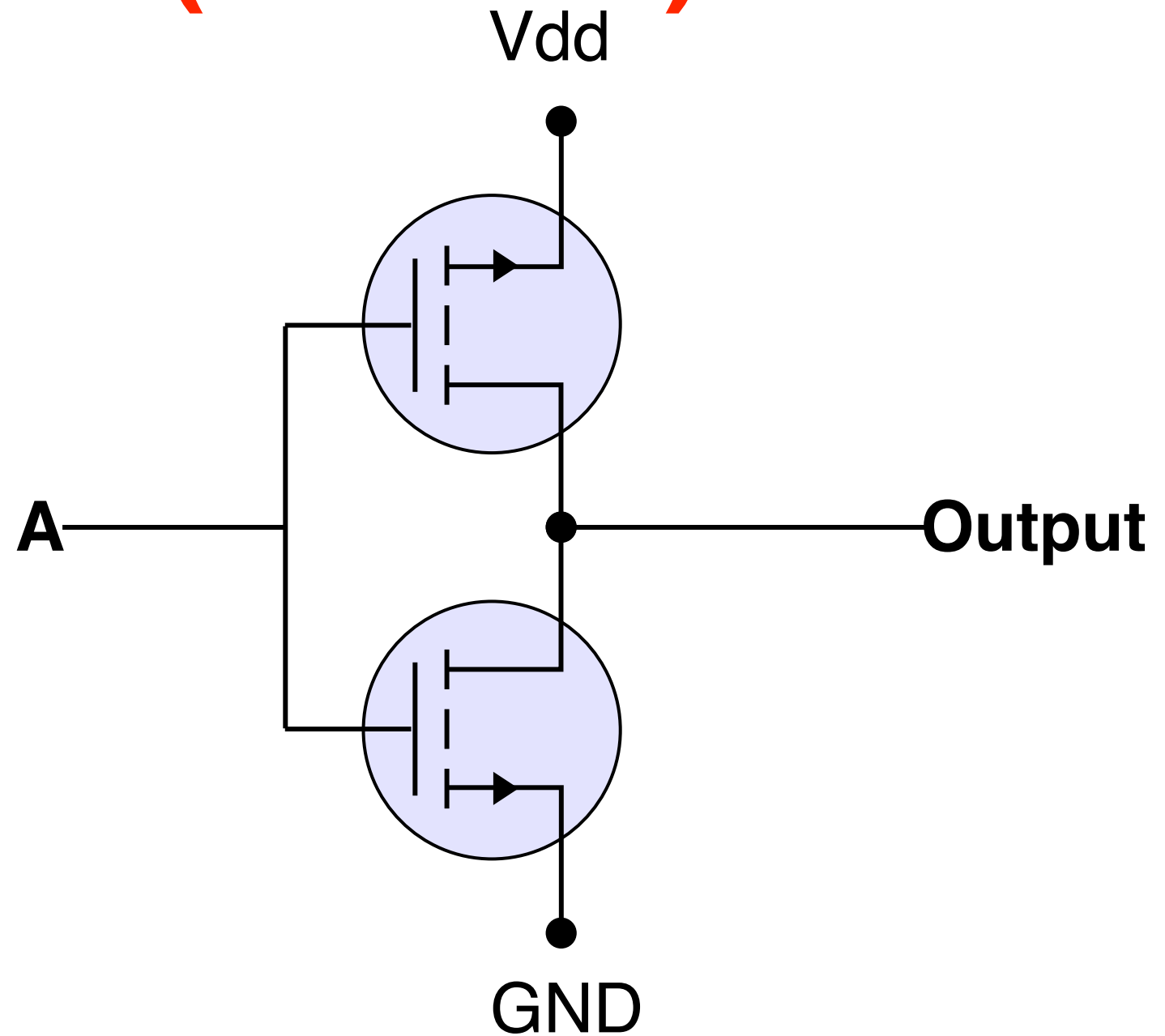





# AND Gate

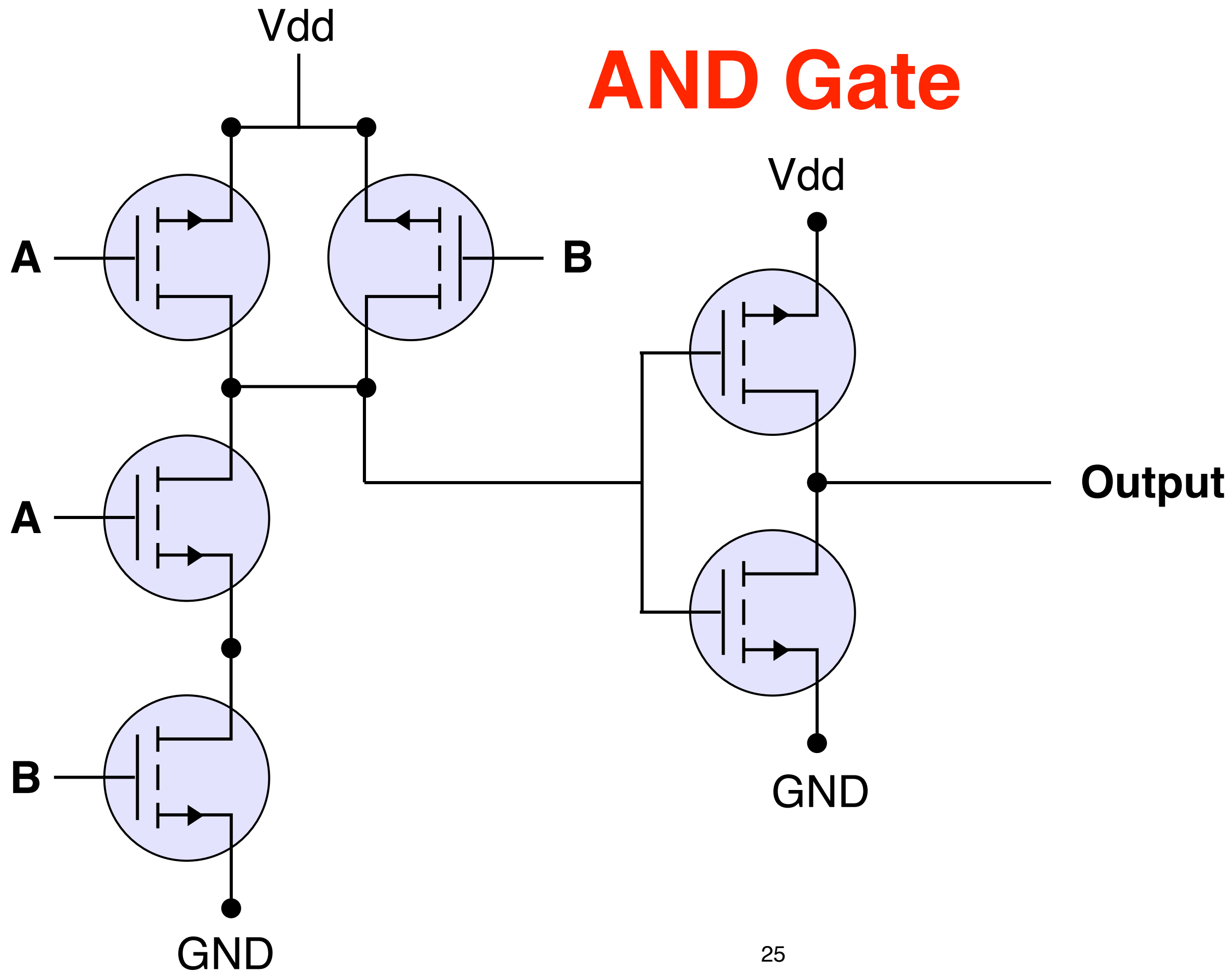

# OR Gate

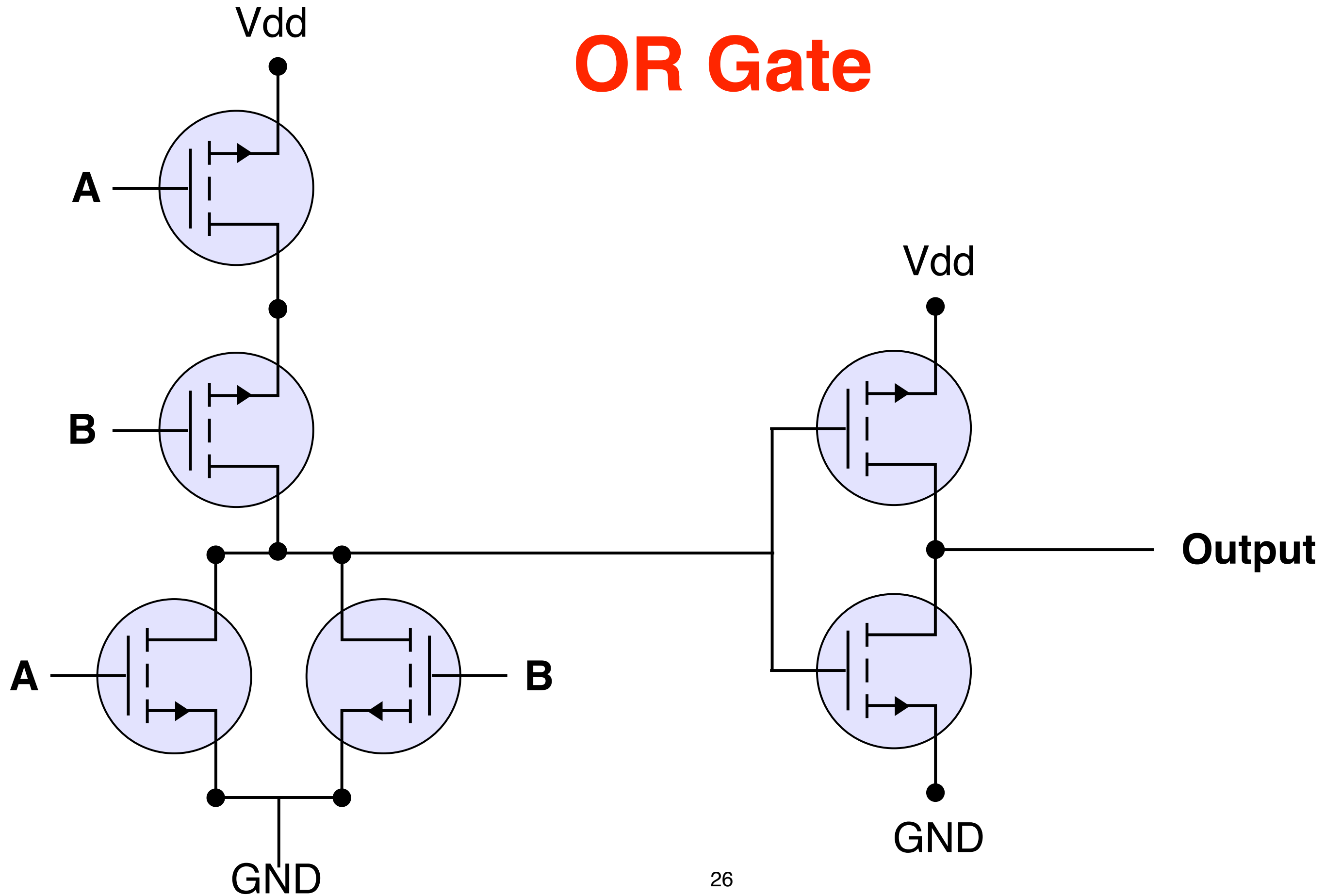

# NAND Gate

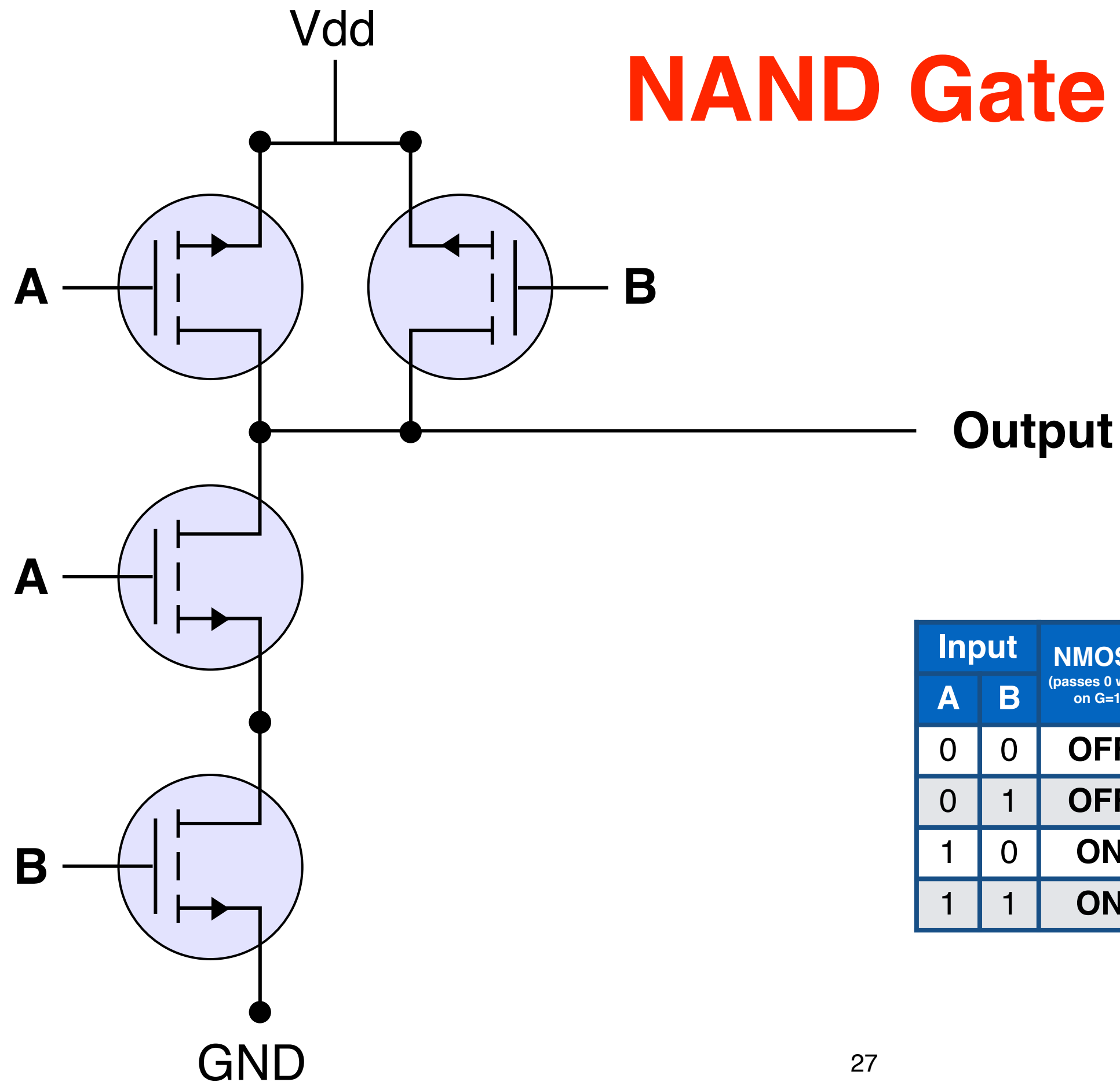


Input		NMOS1 (passes 0 when on G=1)	PMOS1 (passes 1 when on G=0)	NMOS2 (passes 0 when on G=1)	PMOS2 (passes 1 when on G=0)	Output
A	B					
0	0	OFF	ON	OFF	ON	1
0	1	OFF	ON	ON	OFF	1
1	0	ON	OFF	OFF	ON	1
1	1	ON	OFF	ON	OFF	0


# Why use NAND?

- NAND and NOR are “universal gates” — you can build any circuit with everything NAND or NOR
- Simplifies the design as you only need one type of gate
- NAND only needs 4 transistors — gate delay is smaller than OR/AND that needs 6 transistors
- NAND is slightly faster than NOR due to the physics nature

# How about total number of transistors?

 

 
4 gates, each 6 transistors : total 24 transistors



9 gates, each 4 transistors : total 36 transistors
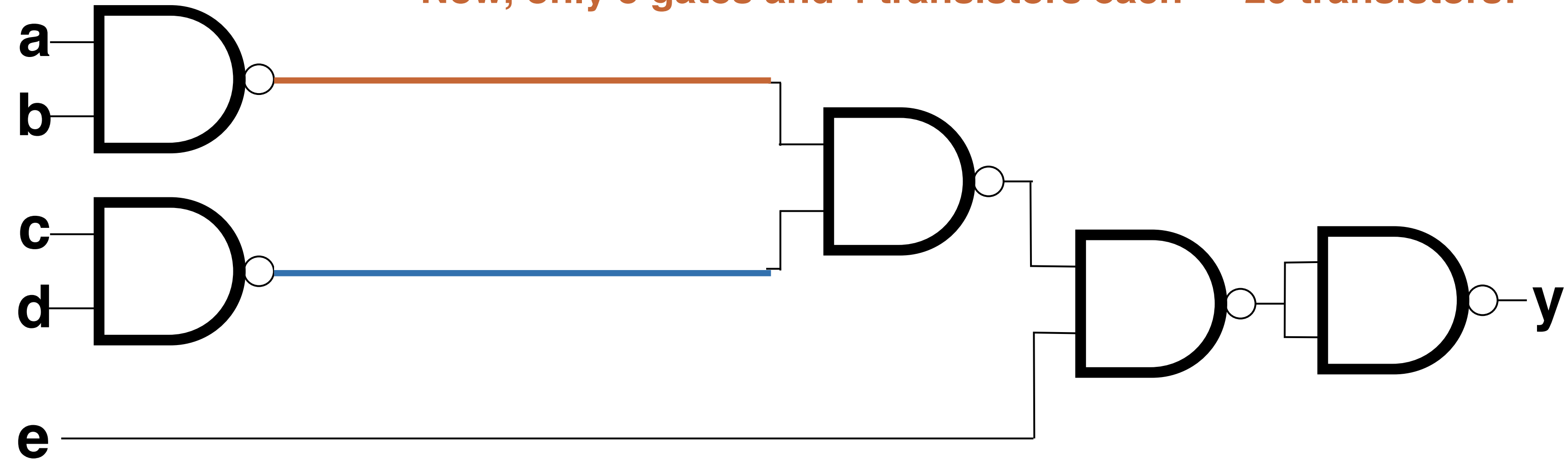
# However ...

Now, only 5 gates and 4 transistors each — 20 transistors!



# How big is the truth table of $y = e(ab+cd)$

- How many rows do we need to express the circuit represented by  $y = e(ab+cd)$ 
  - A. 5
  - B. 9
  - C. 25
  - D. 32
  - E. 64

# How big is the truth table of $y = e(ab+cd)$

- How many rows do we need to express the circuit represented by  $y = e(ab+cd)$

A. 5

B. 9

C. 25

☒ D. 32

E. 64

$$2 \times 2 \times 2 \times 2 \times 2 = 2^5 = 32$$

**Boolean expression is a lot more compact than a truth table!**



# **Can We Get the Boolean Equation from a Truth Table?**

# Definitions of Boolean Function Expressions

- Complement: variable with a bar over it or a ' —  $A'$ ,  $B'$ ,  $C'$
- Literal: variable or its complement —  $A$ ,  $A'$ ,  $B$ ,  $B'$ ,  $C$ ,  $C'$
- Implicant (Product term): product of literals —  $ABC$ ,  $AC$ ,  $BC$
- Implicate (Sum terms): sum of literals —  $(A+B+C)$ ,  $(A+C)$ ,  $(B+C)$
- Minterm: AND that includes all input variables —  $ABC$ ,  $A'BC$ ,  $AB'C$
- Maxterm: OR that includes all input variables —  $(A+B+C)$ ,  $(A'+B+C)$ ,  $(A'+B'+C)$

# Canonical form — Sum of “Minterms”

Input		Output
X	Y	
0	0	0
0	1	0
1	0	1
1	1	1

A minterm

$$f(X,Y) = \underline{XY'} + \underline{XY}$$

Sum (OR) of “product” terms

**XNOR**

Input		Output
A	B	
0	0	1
0	1	0
1	0	0
1	1	1

$$f(A,B) = \underline{A'B'} + \underline{AB}$$

# Canonical form — Product of “Maxterms”

A “maxterm

$$f(X,Y) = (X+Y) (X + Y')$$

← Product of maxterms

Input		Output
X	Y	
0	0	0
0	1	0
1	0	1
1	1	1

**XNOR**

Input		Output
A	B	
0	0	1
0	1	0
1	0	0
1	1	1

$$f(A,B) = (A+B') (A'+B)$$

# Minterms and Maxterms

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

# Sum-of-Products Form

- Represent a function **f** by a **sum of minterms**
- Each **minterm** is **ANDed** with the **value of f**

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$$f = m_1 + m_4 + m_5 + m_6$$

$$= \sum(m_1, m_4, m_5, m_6)$$

$$= \sum m(1, 4, 5, 6)$$

$$= \sum_{x_1, x_2, x_3} (1, 4, 5, 6)$$

$$= x_1'x_2'x_3 + x_1x_2'x_3' + x_1x_2'x_3 + x_1x_2x_3'$$

- A logic expression in the **sum-of-products (SoP)** form:
  - Consisting of product (AND) terms that are summed (ORed)
- **Canonical SoP**: each product term is a **minterm**

# Product-of-Sums Form

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

$f = M_0 M_2 M_3 M_7$   
 $= \Pi (M_0, M_2, M_3, M_7)$   
 $= \Pi M(0, 2, 3, 7)$   
 $= \Pi_{x_1, x_2, x_3} (0, 2, 3, 7)$   
 $= (x_1 + x_2 + x_3)(x_1 + x'_2 + x_3)(x_1 + x'_2 + x'_3)(x'_1 + x'_2 + x'_3)$

- ❑ A logic expression in the **product-of-sums (PoS)** form:
  - Consisting of sum (OR) terms that are the factors of a logical product
- ❑ **Canonical PoS**: each sum term is a **maxterm**

**Let's design a circuit!**



# Binary addition

$$3 + 2 = 5$$

$$\begin{array}{r} \text{1 carry} \\ 0011 \\ + 0010 \\ \hline 0101 \end{array}$$

Input			Output	
A	B	Cin	Out	Cout
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

full adder — adder with  
a carry as an input

$$3 + 3 = 6$$

$$\begin{array}{r} \text{1 1} \\ 0011 \\ + 0011 \\ \hline 0110 \end{array}$$

half adder — adder  
without a carry as an  
input


Input		Output	
A	B	Out	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

# Half adder

Input		Output	
A	B	Out	Cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Out} = A'B + AB'$$

$$\text{Cout} = AB$$

 

# The sum-of-product form of the full adder

- How many of the following minterms are part of the sum-of-product form of the full adder in generating the output bit?

2 Mins Poll

- ①  $A'B'Cin'$
- ②  $A'BCin'$
- ③  $AB'Cin'$
- ④  $ABCin'$
- ⑤  $A'B'Cin$
- ⑥  $A'BCin$
- ⑦  $AB'Cin$
- ⑧  $ABCin$

- A. 0
- B. 1
- C. 2
- D. 3
- E. 4

# The sum-of-product form of the full adder

- How many of the following minterms are part of the sum-of-product form of the full adder in generating the output bit?

①  $A'B'Cin'$

②  $A'BCin'$

③  $AB'Cin'$

④  $ABCin'$

⑤  $A'B'Cin$

⑥  $A'BCin$

⑦  $AB'Cin$

⑧  $ABCin$

A. 0

B. 1

C. 2

D. 3

E. 4

Input			Output	
A	B	Cin	Out	Cout
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

$$\begin{aligned}\text{Out} &= A'BCin' + AB'Cin' + A'B'Cin + ABCin \\ \text{Cout} &= ABCin' + A'BCin + AB'Cin + ABCin\end{aligned}$$

# sum-of-products/product-of-sums

- They can be used interchangeably
- Depends on if the truth table has more 0s or 1s in the result
- Neither forms give you the “optimized” equation. By optimized, we mean — minimize the number of operations

**Can we simplify these  
functions?**

# Sum-of-minterms

- Different equations may represent the same function. Ex:  $y = a + b$ , and  $y = a + a'b$ , represent the same function. The sameness is not obvious, so a standard equation form is desirable.
- A **canonical form** of a Boolean equation is a standard equation form for a function.
- **Sum-of-minterms** form is a canonical form of a Boolean equation where the right-side expression is a **sum-of-products** with each product a unique minterm.
- A **minterm** is a product term having **exactly one literal** for **every** function **variable**.
- A **literal** is a variable appearance, in true or complemented form, in an expression, such as  $b$ , or  $b'$ .

# Laws in Boolean Algebra

	OR	AND
Associative laws	$(a+b)+c=a+(b+c)$	$(a \cdot b) \cdot c=a \cdot (b \cdot c)$
Commutative laws	$a+b=b+a$	$a \cdot b=b \cdot a$
Distributive laws	$a+(b \cdot c)=(a+b) \cdot (a+c)$	$a \cdot (b+c)=a \cdot b+a \cdot c$
Identity laws	$a+0=a$	$a \cdot 1=a$
Complement laws	$a+a'=1$	$a \cdot a'=0$

Duality: We swap all operators between (+,.) and interchange all elements between (0,1). For a theorem if the statement can be proven with the laws of Boolean algebra, then the duality of the statement is also true.



# Some more tools

	OR	AND
DeMorgan's Theorem	$(a + b)' = a'b'$	$a'b' = (a + b)'$
Covering Theorem	$a(a+b) = a+ab = a$	$ab + ab' = (a+b)(a+b') = a$
Consensus Theorem	$ab+ac+b'c = ab+b'c$	$(a+b)(a+c)(b'+c) = (a+b)(b'+c)$
Uniting Theorem	$a (b + b') = a$	$(a+b) \cdot (a+b')=a$
Shannon's Expansion	$f(a,b,c) = a'b' + bc + ab'c$ $f(a,b,c) = a f(1, b, c) + a' f(0,b,c)$	

# Applying Theorems

- Which of the following represents  $CB+BA+C'A$ ?

A.  $AB+AC'$

B.  $BC+AC'$

C.  $AB+BC$

D.  $AB+AC$

E. None of the above

	OR	AND
Associative laws	$(a+b)+c=a+(b+c)$	$(a \cdot b) \cdot c=a \cdot (b \cdot c)$
Commutative laws	$a+b=b+a$	$a \cdot b=b \cdot a$
Distributive laws	$a+(b \cdot c)=(a+b) \cdot (a+c)$	$a \cdot (b+c)=a \cdot b+a \cdot c$
Identity laws	$a+0=a$	$a \cdot 1=a$
Complement laws	$a+a'=1$	$a \cdot a'=0$
DeMorgan's Theorem	$(a+b)'=a'b'$	$a'b'=(a+b)'$
Covering Theorem	$a(a+b)=a+ab=a$	$ab+ab'=(a+b)(a+b')=a$
Consensus Theorem	$ab+ac+b'c=ab+b'c$	$(a+b)(a+c)(b'+c)=(a+b)(b'+c)$
Uniting Theorem	$a(b+b')=a$	$(a+b) \cdot (a+b')=a$
Shannon's Expansion	$f(a,b,c)=a'b'+bc+ab'c$ $f(a,b,c)=a f(1,b,c)+a' f(0,b,c)$	

# Applying Theorems

2 Mins Poll

- Which of the following represents  $BC+BA+C'A$ ?

A.  $AB+AC'$

B.  $BC+AC$

C.  $AB+BC$

D.  $AB+AC$

E. None of the above

Consensus Theorem

$$ab+ac+b'c = ab+b'c$$

$$\begin{aligned} &CB + BA1 + C'A \\ &= BC + BA(C'+C) + C'A \\ &= BC + BAC' + BAC + C'A \\ &= (1+A)BC + (B+1)AC' \\ &= BC + AC' \end{aligned}$$

# How many “OR”s?

- For the truth table shown on the right, what's the minimum number of “OR” gates we need?

- A. 1
- B. 2
- C. 3
- D. 4
- E. 5

Input			Output
A	B	C	
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	0	0	1
1	1	1	0

# How many “OR”s?

- For the truth table shown on the right, what's the minimum number of “OR” gates we need?

A. 1  $F(A, B, C) =$

B. 2  $A'B'C' + A'B'C + A'BC' + A'BC + AB'C' + ABC'$

C. 3  $= A'B'(C'+C) + A'B(C'+C) + AC'(B'+B)$

D. 4  $= A'B' + A'B + AC'$

E. 5  $= A' + AC' = A'(1+C') + AC'$  Distributive Laws  
 $= A' + A'C' + AC'$   
 $= A' + (A'+A)C'$   
 $= A' + C'$

Input			Output
A	B	C	
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0