

University of California Riverside
EE/CS120A-Logic Design-2021 Fall
Instructor: Jia Chen

Homework 2

Submission deadline: Nov. 17th, Wednesday

Problem 1: Manipulate a circuit in Figure 1 so that it uses only NAND gates

 


Figure 1

Problem 2: Using Karnaugh Maps, find a simplest SOP expression for each of the following functions.

1) $F = \sum_{x,y,z}(1,3,5,6,7);$

2) $F = \sum_{w,x,y,z}(0,1,6,7,8,9,14,15);$

3) $F = \prod_{w,x,y}(1,4,5,6,7)$

Problem 3: Using Karnaugh Maps, find a simplest POS expression for each of the following functions.

1) $F = \sum_{w,x,y,z}(0,1,6,7,8,9,14,15);$

2) $F = \prod_{w,x,y}(1,4,5,6,7)$

Problem 4: Sketch the outputs (Q and QN) of an SR-Latch (the basic latch) of the type shown in Figure 4 for the input waveforms shown below Figure 4. Assuming that initially $Q=0$ and $QN=1$.

 


Figure 4: Circuit (a) and characteristic table (b) of SR-Latch



Problem 5: Sketch the Output of a Master-Slave D Flip-flop for the input waveforms shown below. Assuming that initially Output=0.

